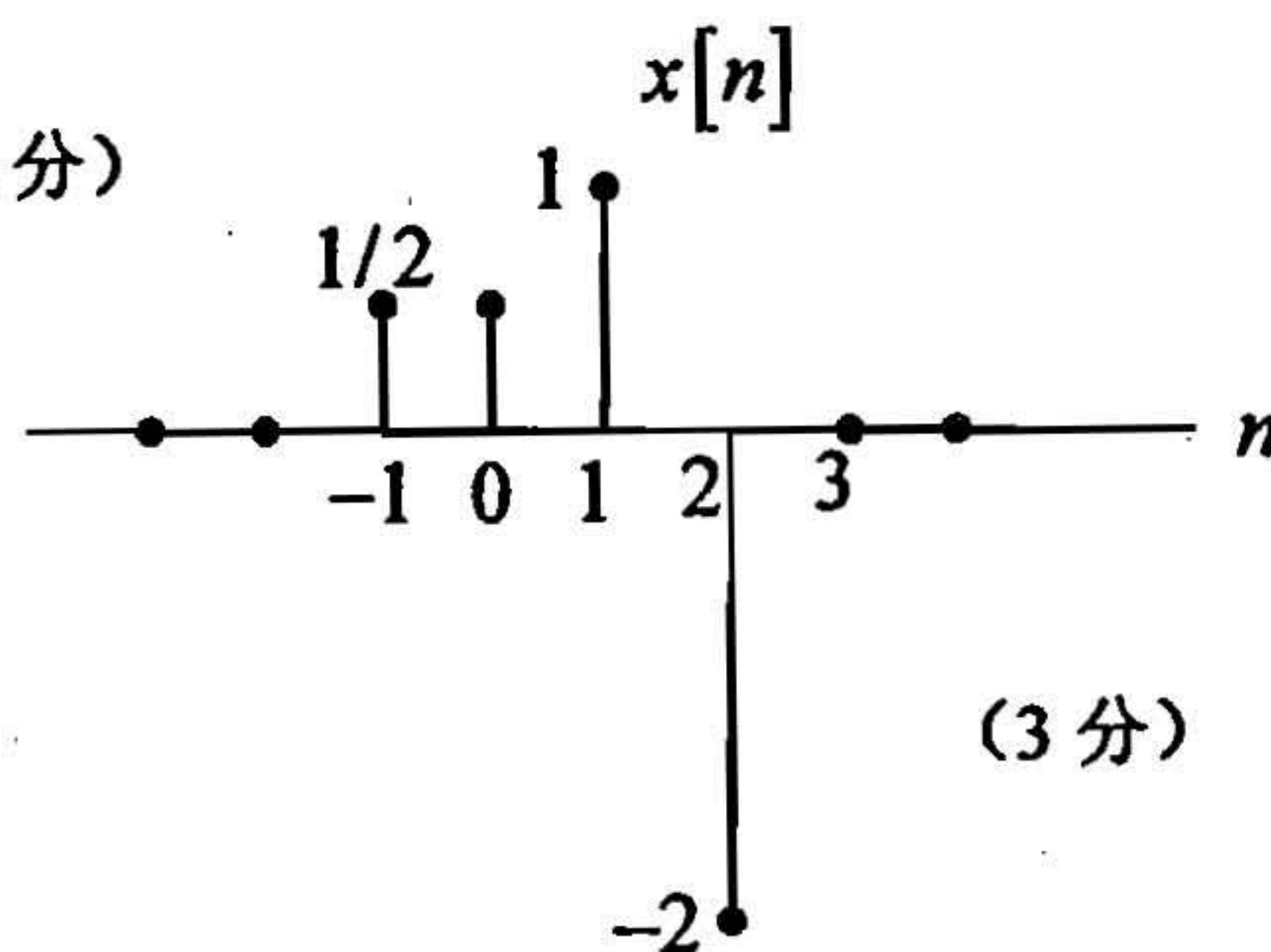


电子科技大学

2008 年攻读硕士学位研究生入学试题参考解答


考试科目：836 信号与系统和数字电路

1. 解: (1) $x[n] = \left\{ \frac{1}{2}, \frac{1}{2}, 1, -2 \right\} \quad n = -1, 0, 1, 2$ (4分)



(3分)

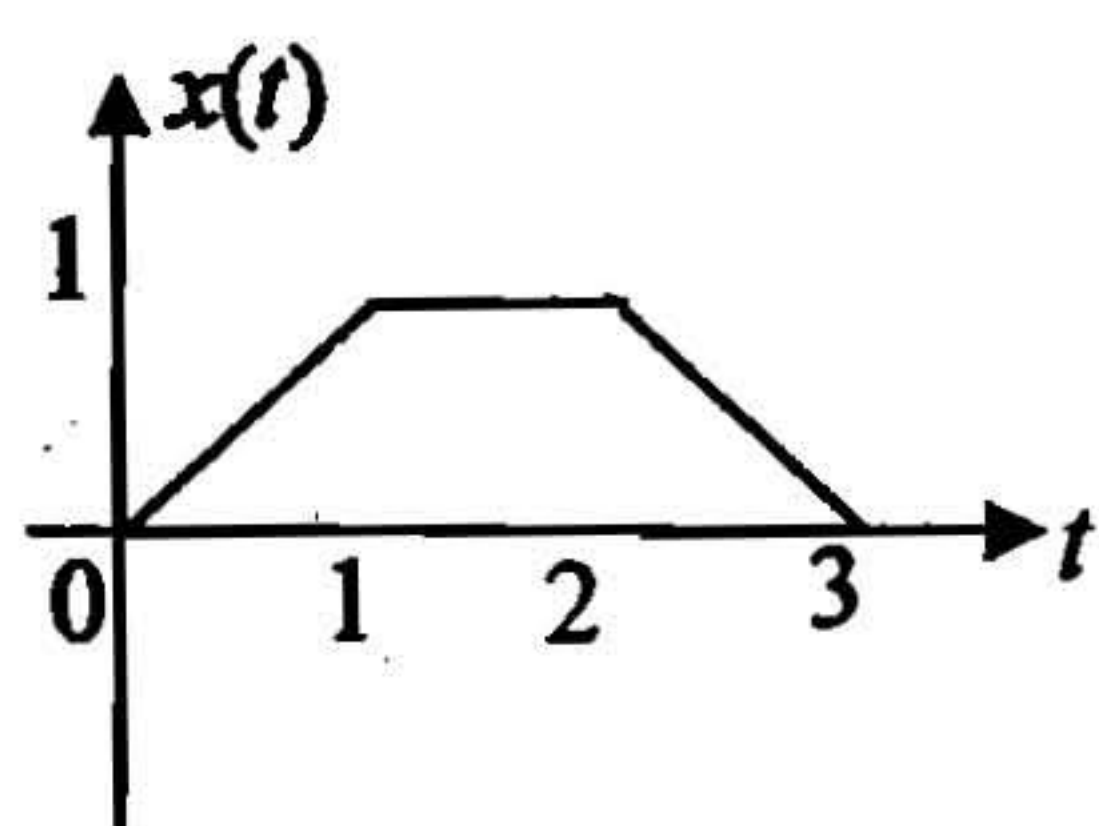(2) $x(t) = tu(t) - (t-1)u(t-1) - (t-2)u(t-2) + (t-3)u(t-3)$ (4分)



(4分)

2. 解:

$$Ev\{x(t)\} \longleftrightarrow \text{Re}\{X(j\omega)\} \quad (4分)$$

$$\text{令 } x_1(t) = u(t+2) - u(t-2), \quad x_2(t) = u(t+1) - u(t-1)$$

$$Ev\{x(t)\} = \frac{3}{2}x_1(t) - \frac{1}{2}x_2(t) \quad (4分)$$

$$\text{Re}\{X(j\omega)\} = \frac{(6\cos\omega - 1)\sin\omega}{\omega} \quad (7分)$$

3. 解:

$$h(t) = h_1(t) - h_2(t) * h_3(t) = \frac{\sin\frac{7\pi}{2}t}{\pi t} - \frac{\sin\frac{3\pi}{2}t}{\pi t} \quad (3分)$$

$$H(j\omega) = \begin{cases} 1 & \frac{3\pi}{2} < |\omega| < \frac{7\pi}{2} \\ 0 & \text{others} \end{cases} \quad (3 \text{ 分})$$

$$x(t) = \sum_{k=-\infty}^{+\infty} a_k e^{jk\pi t} \quad a_k = \frac{1}{2} [1 - (-1)^k] \quad (4 \text{ 分})$$

$$y(t) = \sum_{k=-\infty}^{+\infty} a_k H(jk\pi) e^{jk\pi t} = 2 \cos 3\pi t \quad (5 \text{ 分})$$

4. 解:

$$y(t) = x(t) * \frac{\sin Wt}{\pi t} + [x(t) \cos 2\omega_0 t] * \frac{\sin Wt}{\pi t} \quad (4 \text{ 分})$$

当 $\omega_M < W < 2\omega_0 - \omega_M$ 时可保证 $y(t) = x(t)$ (5 分)

5. 解:

$$(1) H(s) = \frac{1}{(s+1)(s+2)}, \quad \text{Re}\{s\} > -1 \quad (3 \text{ 分})$$

$$(2) h(t) = (e^{-t} - e^{-2t})u(t) \quad (3 \text{ 分})$$

该系统是因果系统。(3 分)

$$(3) y(t) = [(t-1)e^{-t} + e^{-2t}]u(t) \quad (4 \text{ 分})$$

$$(4) \frac{d^2}{dt^2} y(t) + 3 \frac{d}{dt} y(t) + 2y(t) = x(t) \quad (3 \text{ 分})$$


6. 解:

$$(1) H(z) = \frac{z^{-2}}{(1 - \frac{1}{2}z^{-1})^2} \quad |z| > \frac{1}{2} \quad (2 \text{ 分})$$


$z = \frac{1}{2}$ 处有一个二阶极点 (2 分)

$$(2) h[n] = 4(n-1) \left(\frac{1}{2}\right)^n u[n-2] \quad (2 \text{ 分})$$

该系统是稳定的。(2 分)

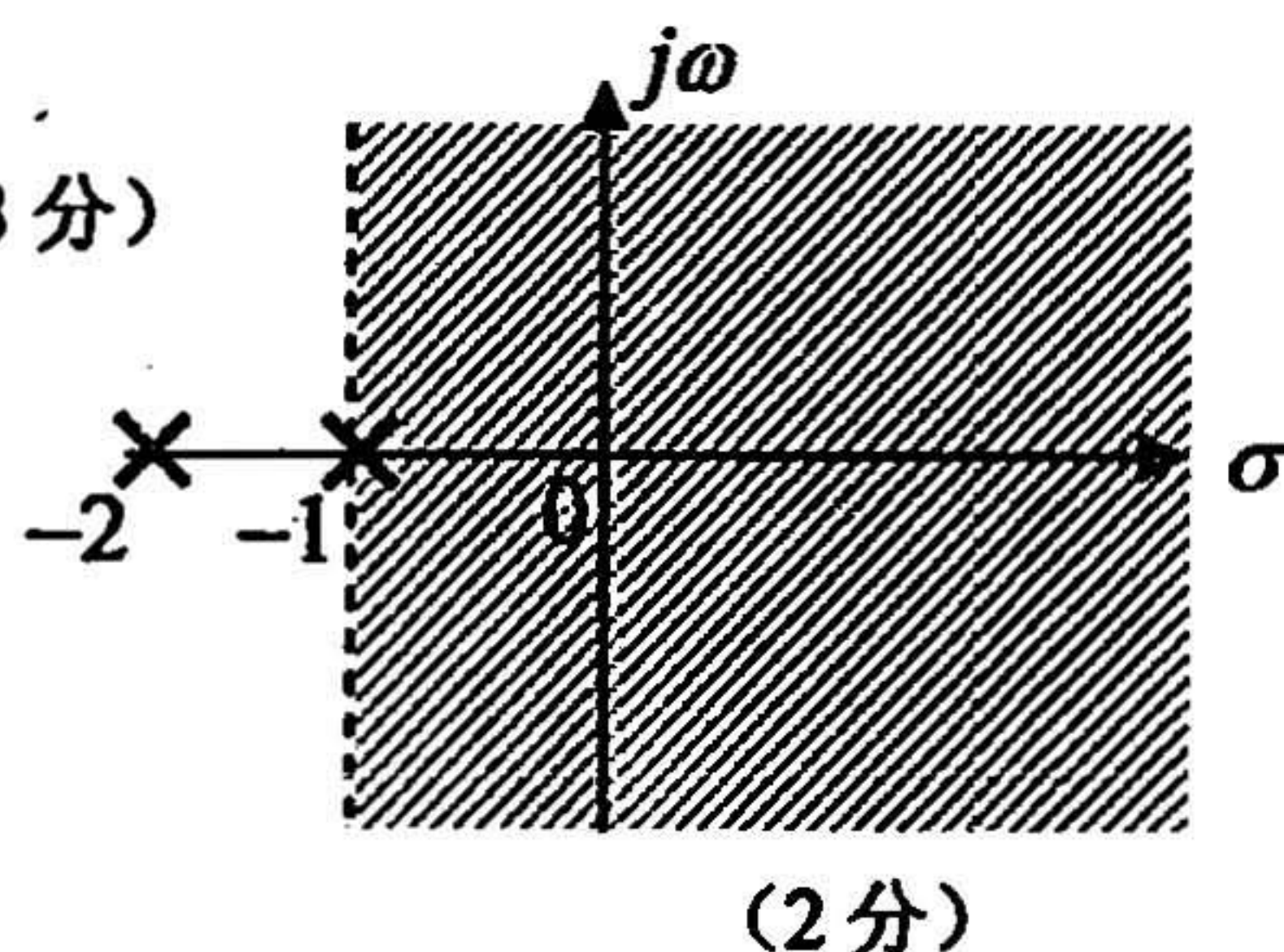


(2 分)

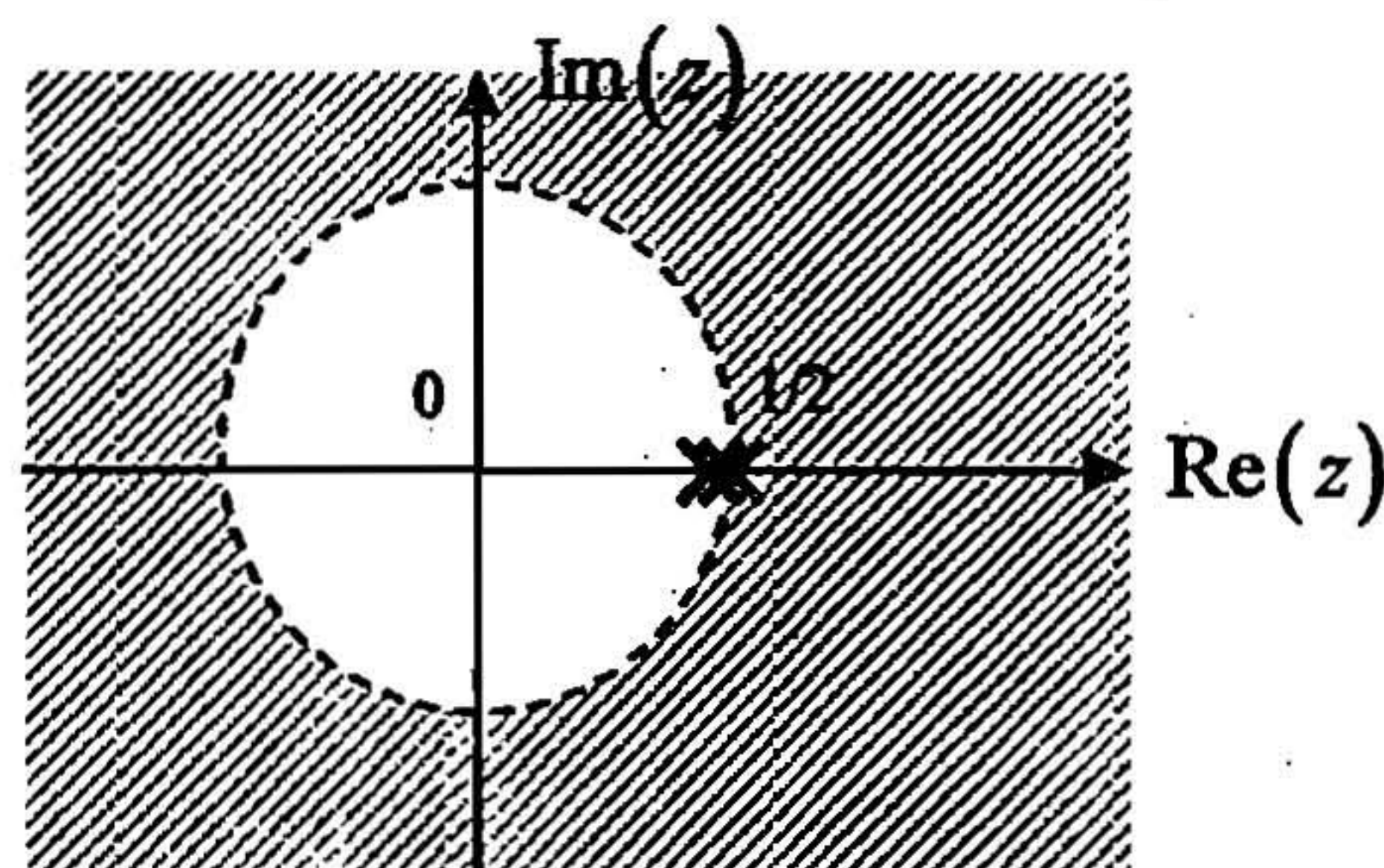

(2 分)

(3) $y[n] = \frac{4}{9} \cos \pi n$ (4分)

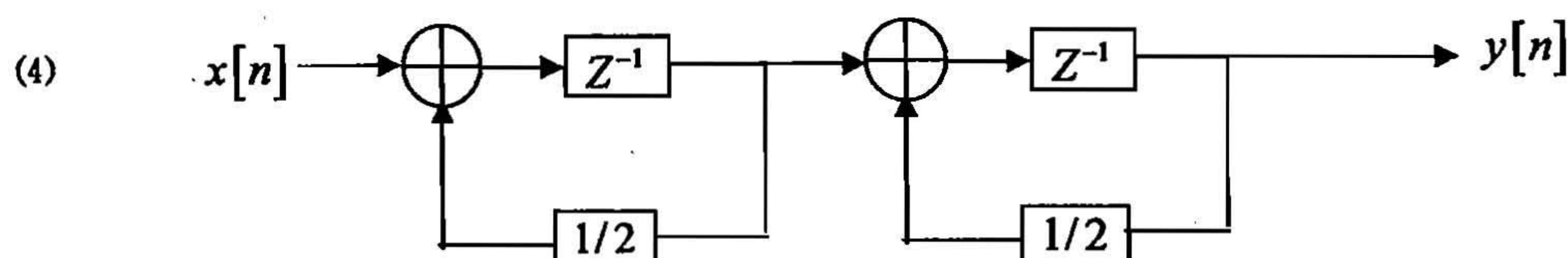

(4分)

7. 填空 (每小题 4 分, 共 20 分)

- (1). (100011. 001) (23. 2)
 (2). (11010011) (11010010)
 (3). (1011001)
 (4). (8)
 (5). $\prod_{ABCD} (2,4,5,7,9,14)$

8. 组合设计

(1). (10分)

M	A	B	Cin	S	Cout
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	1	1
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	1	1
1	1	0	1	0	1
1	1	1	0	0	0
1	1	1	1	1	1

$$S = \sum_{MABCin} (1,2,4,7,9,10,12,15) = \overline{A}B\overline{C}in + A\overline{B}Cin + \overline{A}B\overline{C} + \overline{A}B\overline{C} = A \oplus B \oplus Cin$$

$$Cout = \sum_{MABCin} (3,5,6,7,9,12,13,15) = ACin + M\overline{A}\overline{B} + M\overline{B}C + \overline{M}BC + \overline{M}AB$$

(2). A,B,C 分别接 C3,C2,C1, 则 S0=S2=S4=S6=1, S5=S7=0 电平, S1=D', S3=D (5 分)

9. (10 分)

$$D_2 = \overline{Q_2}Q_1x, D_1 = \overline{x} + \overline{Q_2}Q_1, Z = Q_2x$$

Q2	Q1	X	Q2*	Q1*	Z
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	0	1	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	0	1	0
1	1	1	0	0	1

10.

(1). $D_2 = (Q_1 \oplus Q_2 \oplus x)', D_1 = \overline{Q_1}$ (8 分)

(2). (7 分)

状态 S	新状态 / 输出	
	X=0	X=1
A	B/0	C/0
B	D/0	E/0
C	E/0	F/0
D	G/0	H/0
E	H/0	I/0
F	I/0	I/0
G	A/0	A/0
H	A/0	A/1
I	A/1	A/1